

Laboratory Exercise 9

A Simple Processor

Figure 1 shows a digital system that contains a number of 9-bit registers, a multiplexer, an adder/subtractor unit, and a control unit(finite state machine). Data is input to this system via the 9-bit *DIN* input. This data can be loaded through the 9-bit wide multiplexer into the various registers, such as *R0*, \dots , *R7* and *A*. The multiplexer also allows data to be transferred from one register to another. The multiplexer's output wires are called a *bus* in the figure because this term is often used for wiring that allows data to be transferred from one location in a system to another.

Addition or subtraction is performed by using the multiplexer to first place one 9-bit number onto the bus wires and loading this number into register *A*. Once this is done, a second 9-bit number is placed onto the bus, the adder/subtractor unit performs the required operation, and the result is loaded into register *G*. The data in *G* can then be transferred to one of the other registers as required.

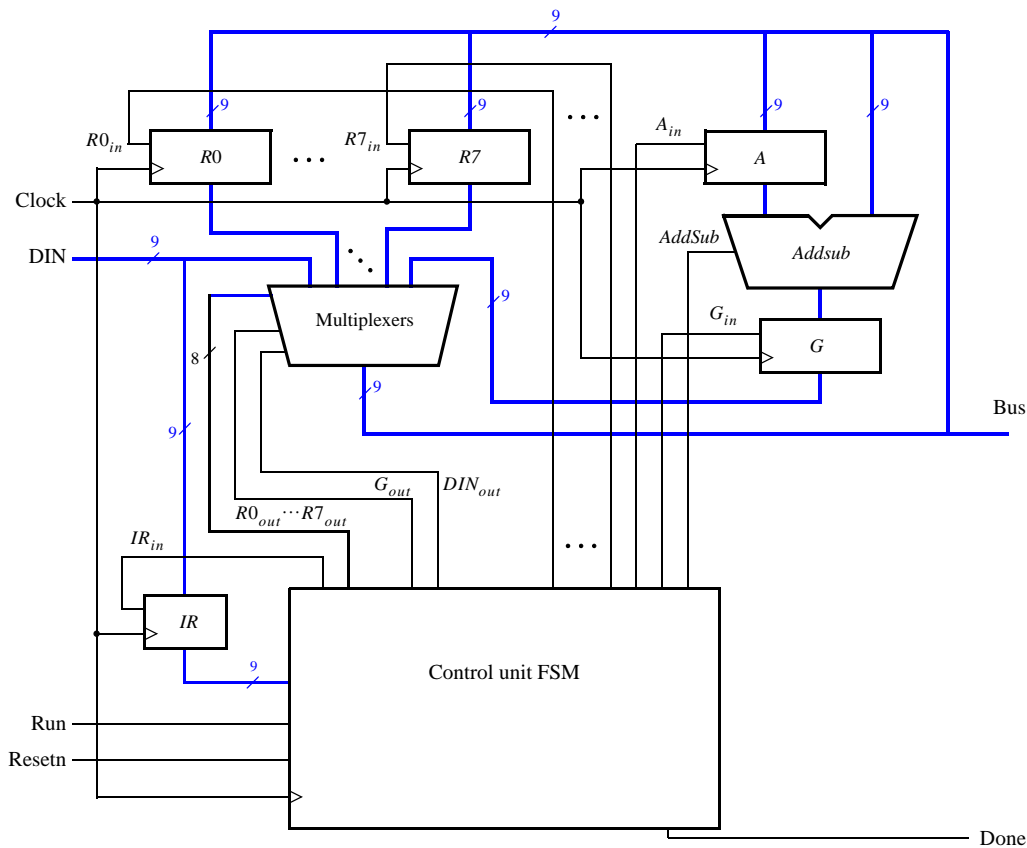


Figure 1: A digital system.

The system can perform different operations in each clock cycle, as governed by the *control unit*. This unit determines when particular data is placed onto the bus wires and it controls which of the registers is to be loaded with this data. For example, if the control unit asserts the signals *R0_out* and *A_in*, then the multiplexer will place the contents of register *R0* onto the bus and this data will be loaded by the next active clock edge into register *A*.

A system like this is often called a *processor*. It executes operations specified in the form of instructions. Table 1

lists the instructions that the processor has to support for this exercise. The left column shows the name of an instruction and its operand. The meaning of the syntax $Rx \leftarrow [Ry]$ is that the contents of register Ry are loaded into register Rx . The **mv** (move) instruction allows data to be copied from one register to another. For the **mvi** (move immediate) instruction the expression $Rx \leftarrow D$ indicates that the 9-bit constant D is loaded into register Rx .

Operation	Function performed
mv Rx, Ry	$Rx \leftarrow [Ry]$
mvi $Rx, \#D$	$Rx \leftarrow D$
add Rx, Ry	$Rx \leftarrow [Rx] + [Ry]$
sub Rx, Ry	$Rx \leftarrow [Rx] - [Ry]$

Table 1: Instructions performed in the processor.

Each instruction can be encoded and stored in the IR register using the 9-bit format $III\text{XXXX}YYY$, where III represents the instruction, XXX gives the Rx register, and YYY gives the Ry register. Although only two bits are needed to encode our four instructions, we are using three bits because other instructions will be added to the processor in later parts of this exercise. Instructions are loaded from an external source, hence IR has to be connected to the nine bits of the DIN input, as indicated in Figure 1. For the **mvi** instruction the YYY field has no meaning, and the immediate data $\#D$ has to be supplied on the 9-bit DIN input after the **mvi** instruction word is stored into IR .

Some instructions, such as an addition or subtraction, take more than one clock cycle to complete, because multiple transfers have to be performed across the bus. The finite state machine in the control unit “steps through” such instructions, asserting the control signals needed in successive clock cycles until the instruction has completed. The processor starts executing the instruction on the DIN input when the *Run* signal is asserted and the processor asserts the *Done* output when the instruction is finished. Table 2 indicates the control signals that can be asserted in each time step to implement the instructions in Table 1. Note that the only control signal asserted in time step 0 is IR_{in} , so this time step is not shown in the table.

	T_1	T_2	T_3
(mv): I_0	$RY_{out}, RX_{in},$ <i>Done</i>		
(mvi): I_1	$DIN_{out}, RX_{in},$ <i>Done</i>		
(add): I_2	RX_{out}, A_{in}	RY_{out}, G_{in}	$G_{out}, RX_{in},$ <i>Done</i>
(sub): I_3	RX_{out}, A_{in}	$RY_{out}, G_{in},$ <i>AddSub</i>	$G_{out}, RX_{in},$ <i>Done</i>

Table 2: Control signals asserted in each instruction/time step.

Part I

Design and implement the processor shown in Figure 1 using Verilog code as follows:

1. Create a new Quartus II project for this exercise.
2. Generate the required Verilog file, include it in your project, and compile the circuit. A suggested skeleton of the Verilog code is shown in parts *a* and *b* of Figure 2, and some subcircuit modules that can be used in this code appear in Figure 2*c*.
3. Use functional simulation to verify that your code is correct. An example of the output produced by a functional simulation for a correctly-designed circuit is given in Figure 3. It shows the value $(040)_{16}$ being loaded into *IR* from *DIN* at time 30 ns. This pattern (the leftmost bits of *DIN* are connected to *IR*) represents the instruction **mvi** *R0*,#*D*, where the value $D = 5$ is loaded into *R0* on the clock edge at 50 ns. The simulation then shows the instruction **mv** *R1*,*R0* at 90 ns, **add** *R0*,*R1* at 110 ns, and **sub** *R0*,*R0* at 190 ns. Note that the simulation output shows *DIN* as a 3-digit hexadecimal number, and it shows the contents of *IR* as a 3-digit octal number.
4. Create a new Quartus II project which will be used for implementation of the circuit on your Altera DE-series board. This project should consist of a top-level module that contains the appropriate input and output ports for the Altera board. Instantiate your processor in this top-level module. Use switches SW_{8-0} to drive the *DIN* input port of the processor and use switch SW_9 to drive the *Run* input. Also, use push button KEY_0 for *Resetn* and KEY_1 for *Clock*. Connect the processor bus wires to $LEDR_{8-0}$ and connect the *Done* signal to $LEDR_9$.
5. Add to your project the necessary pin assignments for your DE-series board. Compile the circuit and download it into the FPGA chip.
6. Test the functionality of your design by toggling the switches and observing the LEDs. Since the processor's clock input is controlled by a push button switch, it is easy to step through the execution of instructions and observe the behavior of the circuit.

```
module proc (DIN, Resetn, Clock, Run, Done, BusWires);  
  input [8:0] DIN;  
  input Resetn, Clock, Run;  
  output Done;  
  output [8:0] BusWires;  
  
  parameter T0 = 2'b00, T1 = 2'b01, T2 = 2'b10, T3 = 2'b11;  
  ... declare variables  
  
  assign I = IR[1:3];  
  dec3to8 decX (IR[4:6], 1'b1, Xreg);  
  dec3to8 decY (IR[7:9], 1'b1, Yreg);
```

Figure 2: Skeleton Verilog code for the processor. (Part *a*)

```

// Control FSM state table
always @(Tstep_Q, Run, Done)
begin
    case (Tstep_Q)
        T0: // data is loaded into IR in this time step
            if (!Run) Tstep_D = T0;
            else Tstep_D = T1;
        T1: ...
    endcase
end

// Control FSM outputs
always @(Tstep_Q or I or Xreg or Yreg)
begin
    ... specify initial values
    case (Tstep_Q)
        T0: // store DIN in IR in time step 0
            begin
                IRin = 1'b1;
            end
        T1: //define signals in time step 1
            case (I)
                ...
            endcase
        T2: //define signals in time step 2
            case (I)
                ...
            endcase
        T3: //define signals in time step 3
            case (I)
                ...
            endcase
    endcase
end

// Control FSM flip-flops
always @(posedge Clock, negedge Resetn)
    if (!Resetn)
        ...

regn reg_0 (BusWires, Rin[0], Clock, R0);
... instantiate other registers and the adder/subtractor unit

... define the bus

endmodule

```

Figure 2: Skeleton Verilog code for the processor. (Part *b*)

```

module dec3to8(W, En, Y);
    input [2:0] W;
    input En;
    output [0:7] Y;
    reg [0:7] Y;

    always @(W or En)
    begin
        if (En == 1)
            case (W)
                3'b000: Y = 8'b10000000;
                3'b001: Y = 8'b01000000;
                3'b010: Y = 8'b00100000;
                3'b011: Y = 8'b00010000;
                3'b100: Y = 8'b00001000;
                3'b101: Y = 8'b00000100;
                3'b110: Y = 8'b00000010;
                3'b111: Y = 8'b00000001;
            endcase
        else
            Y = 8'b00000000;
        end
    endmodule

module regn(R, Rin, Clock, Q);
    parameter n = 9;
    input [n-1:0] R;
    input Rin, Clock;
    output [n-1:0] Q;
    reg [n-1:0] Q;

    always @(posedge Clock)
        if (Rin)
            Q <= R;
    endmodule

```

Figure 2: Subcircuit modules for use in the processor. (Part *c*)

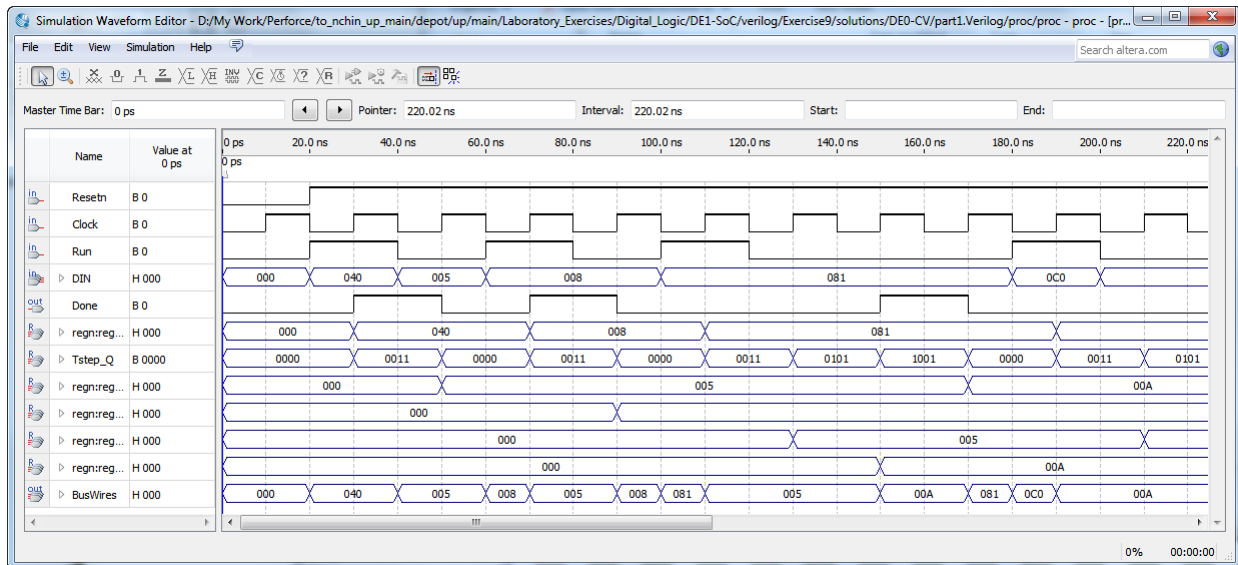


Figure 3: Simulation of the processor.

Part II

In this part you are to design the circuit depicted in Figure 4, in which a memory module and counter are connected to the processor from Part I. The counter is used to read the contents of successive addresses in the memory, and this data is provided to the processor as a stream of instructions. To simplify the design and testing of this circuit we have used separate clock signals, *PClock* and *MClock*, for the processor and memory.

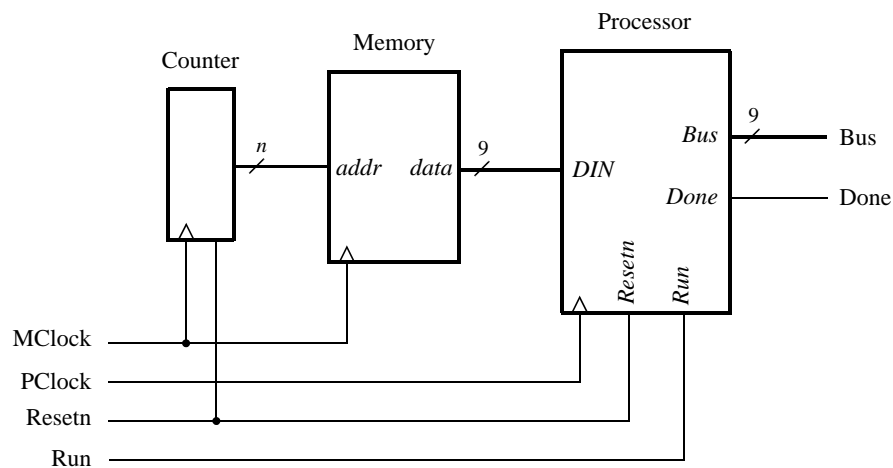


Figure 4: Connecting the processor to a memory and counter.

1. Create a new Quartus II project which will be used to test your circuit.
2. Generate a top-level Verilog file that instantiates the processor, memory, and counter. Use the Quartus II IP Catalog tool to create the memory module, following the procedure that is provided in Laboratory Exercise 8. The correct module is found under the *Basic Functions > On Chip Memory* category and is called *ROM: 1-PORT*. Follow the instructions provided by the wizard to create a memory that has one 9-bit wide read data port and is 32 words deep. Figure 5 and Figure 6 show the relevant pages of the wizard

and how to properly configure the memory. Since this memory has only a read port, and no write port, it is called a *synchronous read-only memory (synchronous ROM)*. Note that the memory includes a register for synchronously loading addresses. This register is required due to the design of the memory resources on the Cyclone series of FPGAs, as was discussed in Laboratory Exercise 8.

To place processor instructions into the memory, you need to specify *initial values* that should be stored in the memory once your circuit has been programmed into the FPGA chip. This can be done by telling the wizard to initialize the memory using the contents of a *memory initialization file (MIF)*. The appropriate screen of the wizard is illustrated in Figure 7. We have specified a file named *inst_mem.mif*, which then has to be created in the directory that contains the Quartus II project. An example of a memory initialization file was provided in Laboratory Exercise 8. You can also use the Quartus II on-line Help to learn about the format of the *MIF* file. Set the contents of your *MIF* file such that it provides enough processor instructions to test your circuit.

3. Use functional simulation to test the circuit. Ensure that data is read properly out of the ROM and executed by the processor.
4. Make sure your project includes the necessary port names and pin location assignments to implement the circuit on your DE-series board. Use switch *SW₉* to drive the processor's *Run* input, use *KEY₀* for *Resetn*, use *KEY₁* for *MClock*, and use *KEY₂* for *PClock*. Connect the processor bus wires to *LEDR₈₋₀* and connect the *Done* signal to *LEDR₉*.
5. Compile the circuit and download it into the FPGA chip.
6. Test the functionality of your design by toggling the switches and observing the LEDs. Since the circuit's clock inputs are controlled by push button switches, it is easy to step through the execution of instructions and observe the behavior of the circuit.

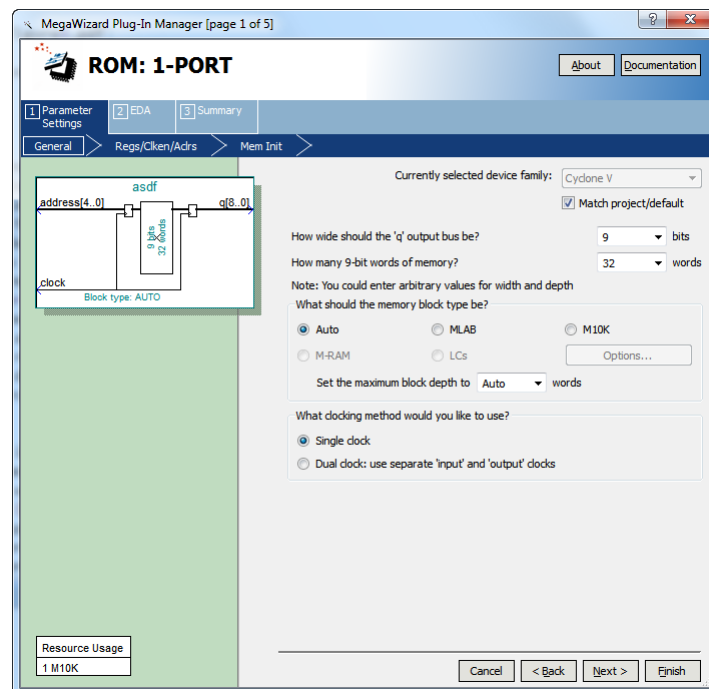


Figure 5: Specifying memory size.

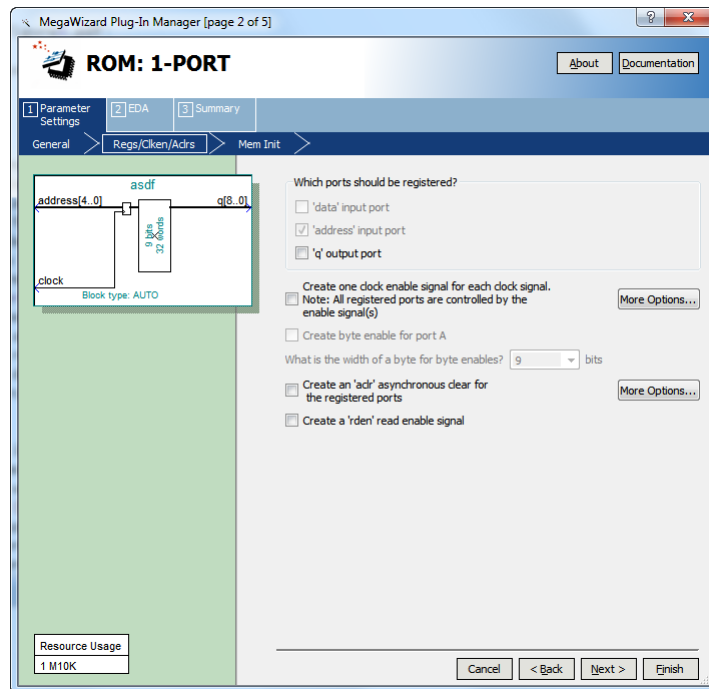


Figure 6: Specifying which memory ports are registered.

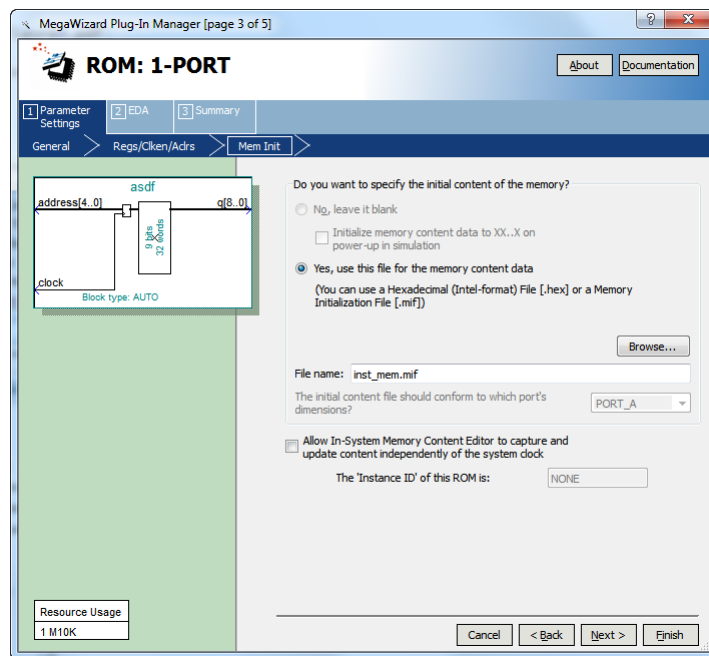


Figure 7: Specifying a memory initialization file (MIF).

Enhanced Processor

It is possible to enhance the capability of the processor so that the counter in Figure 4 is no longer needed, and so that the processor has the ability to perform read and write operations using memory or other devices. These enhancements involve adding new instructions to the processor and the programs that the processor executes are therefore more complex; they are described in Laboratory Exercise 10.

Copyright ©2015 Altera Corporation.